

Reagan Hardy  
Beta Release Phase B  
Embedded Systems Programming  
Dr. Goncalo Martins  
08 June 2023

## Project Requirements

- Cost
  - The cost was not given by the customer.
- Size/aesthetic
  - The final size of the PCB should not exceed 10cm x 10cm.
- Display screen?
  - A seven-segment display will be used to output numbers.
- Time limit
  - Due to the constraints of the given website, the time should not exceed 59 hours and 59 minutes.
- Alarm sound
  - A buzzer will be used to create an alarm like sound.
- Amount of LEDs
  - Two LEDs will be used on the PCB.
- Amount of buttons
  - Two user buttons will be used. One will start the time whereas the other will stop the time.
- Debounce done in software?
  - The buttons will need to have a debounce. This problem was tackled in the software.
- Active or passive buzzer? Or both?
  - An active buzzer was used in KiCad. This means it is polarized.
- Shift register to interface seven segment display
  - The shift register that was used is 74HC595.
- How is it powered?
  - The timer is powered using a USB that connects to a laptop.

## System Design

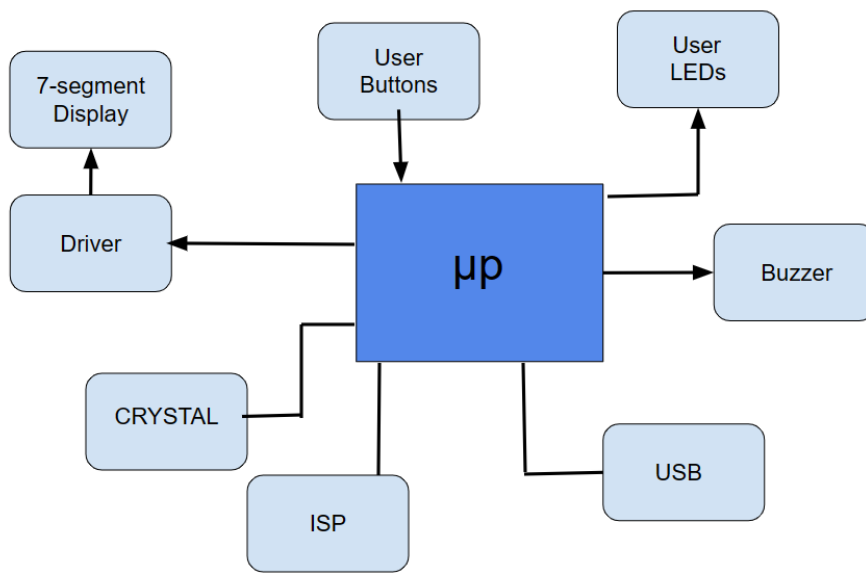


Image 1. The First Design of the Block Diagram

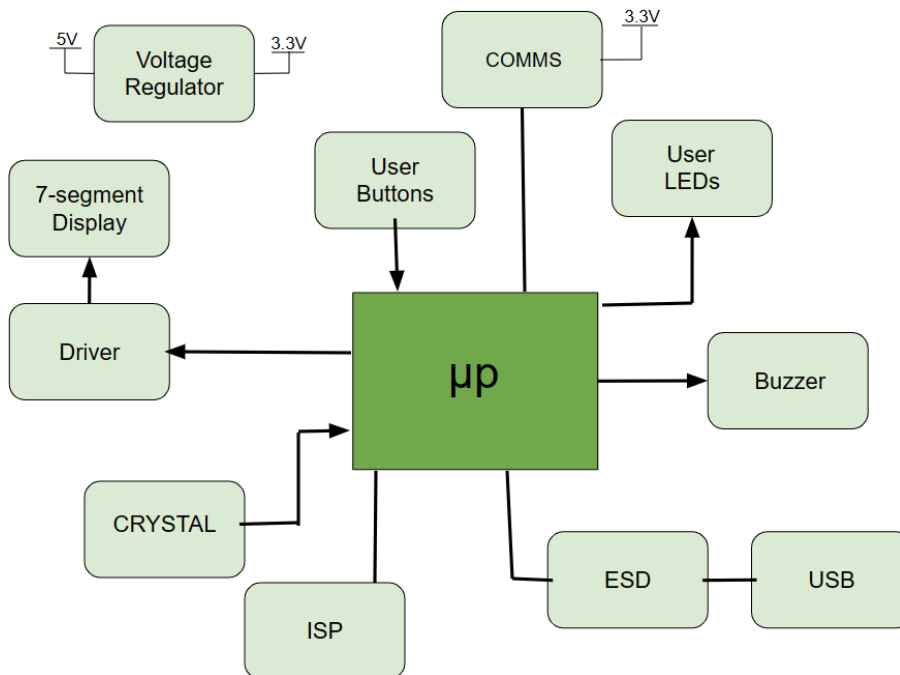


Image 2. The Second Design of the Block Diagram

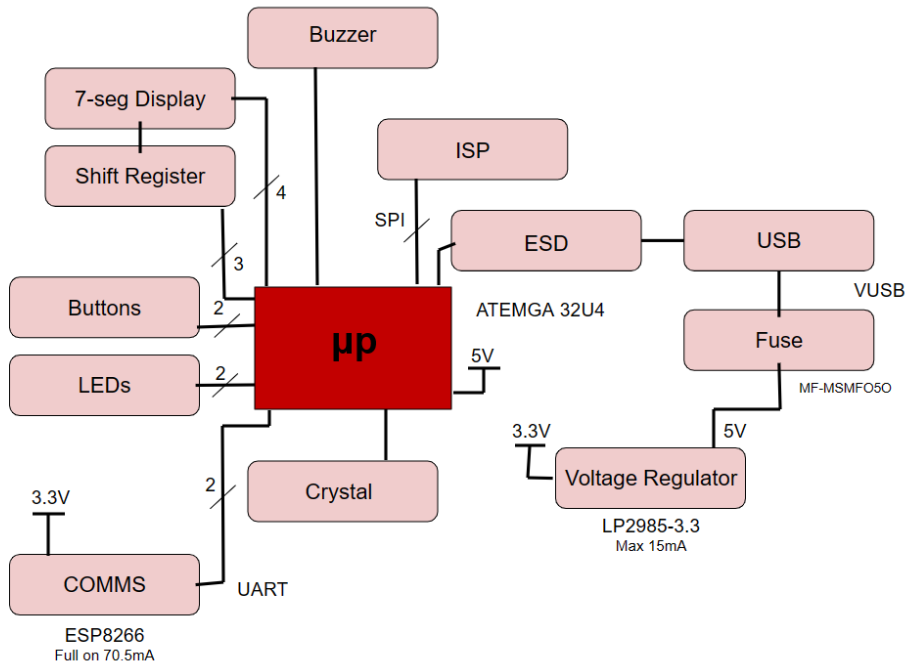


Image 3. The Final Design of the Block Diagram

Throughout the design process, three different block diagrams were created. They linearly improved throughout the lab as more information was considered. The final design was used to create the schematic in KiCad. These diagrams were very important in the design process because they show the entire system in a simple and visually appealing way.

## Components Selection

- Arduino Uno (Optional) / Arduino Mega (Preference) Qt: 1
- 7-Segment Display (Sparkfun) (\$1.60) Qt: 1
- Shift Register 8-Bit (SN74HC595) (Sparkfun) (\$1.05) Qt: 1
- Buttons (Sparkfun) (\$0.55/unit) Qt: 2
- LEDs Qt: 2
- Resistors
- Capacitors
- Mini Speaker (Sparkfun) (\$2.10)
- ESP8266 (Amazon) (\$9 for 3 units)
- Voltage Regulator

Most of these parts were carried over from Phase A. This made the component selection a simple process. It resulted in a cost of less than \$60. This is an important step because the data for these parts can easily be found and stored for future use.

## Build Prototype

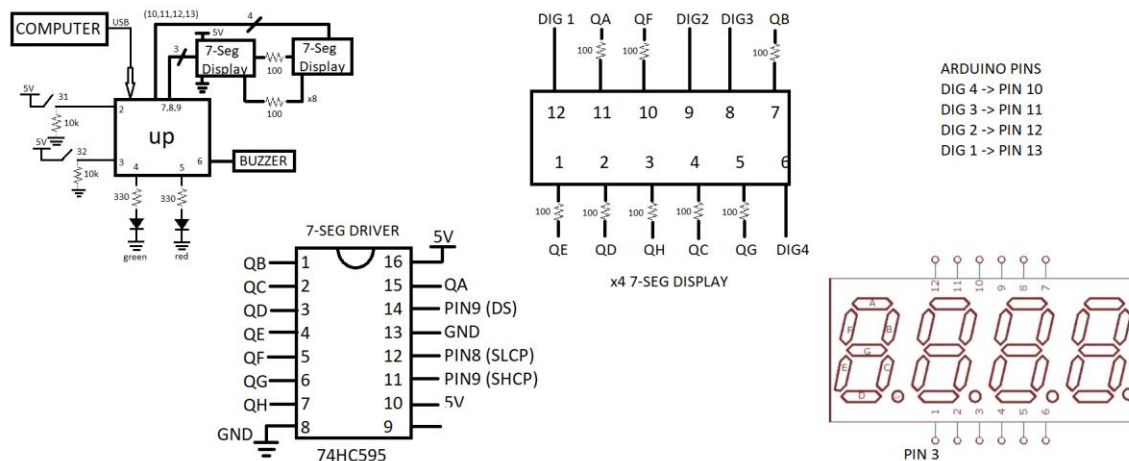


Image 4. Arduino Uno Schematic

During this Phase, an Arduino Shield will be used in conjunction with the created PCB. Arduino Shields provides hardware and controller. The board itself sends commands to the shield. The shield then reacts based on what it was told to do. They communicate via SPI in this case. By using this, it provides ease of use. However, a schematic was drawn out so that there are visuals on pin connections. This came in handy when designing the whole schematic on KiCad.

## PCB Design

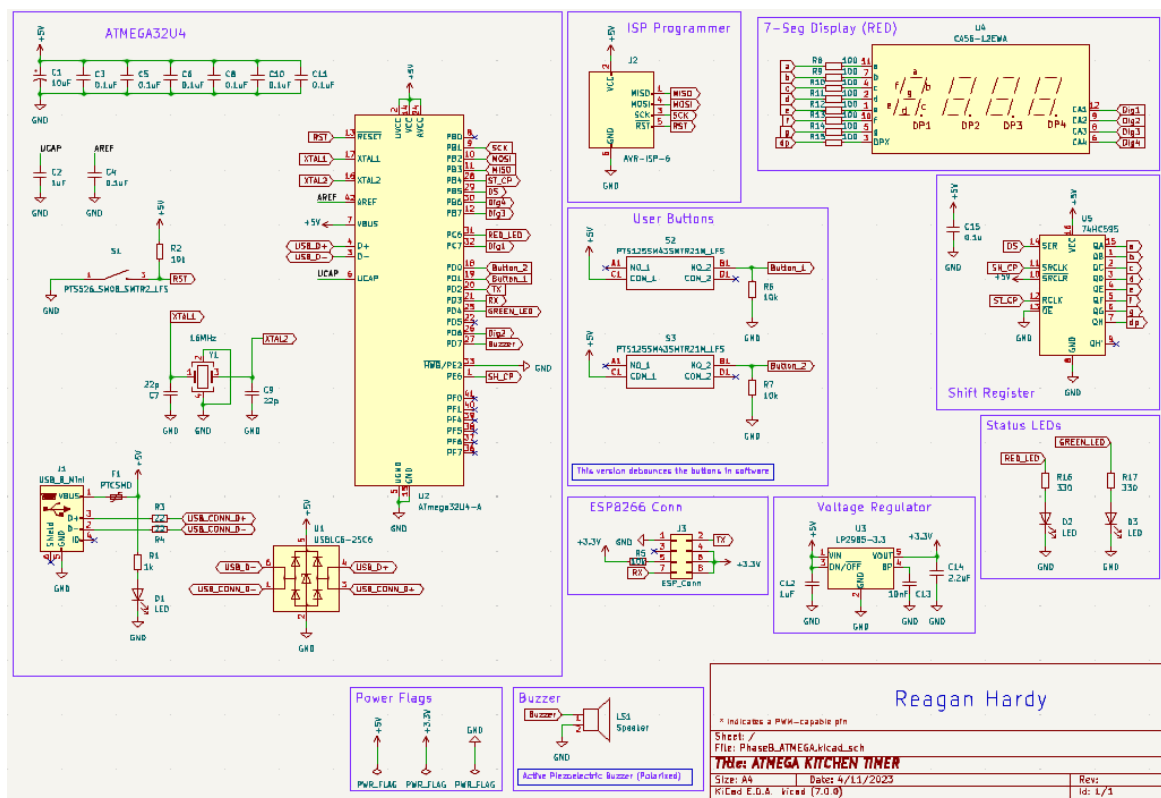


Image 5. Whole Atmega Kitchen Timer Schematic

This was designed using KiCad. To build this, many images were used including images 3 and 4. The components that were built are ATMEGA32U4, power flags, buzzer, ESP8266 Conn, voltage regulator, status LEDs, user buttons, shift register, ISP programmer, and a 7-segment display. Resistors, capacitors, ground, and switches were also used.

 


Image 6. PCB Layout

This layout was taken after the whole process was finished. This includes designing, routing, and labeling. The red lines are on the top plane of copper. Whereas the blue lines are beneath the plane. This helps so that the routes do not cross one another. Labels were added to help with clarity and to add a name and date.

 


Image 7. Front of the Atmega Board

 


Image 8. Back of the Atmega Board

Images 7 and 8 show both sides of the Atmega board. The board itself could not be bigger than 10cm x 10cm. This board is 7cm x 9cm and in a rectangular shape. The 7-segmet display is at the top of the board to eliminate any distractions and to be clearly visible. The USB is on the left-hand side of the board. This was done so that the cable wouldn't be in the way or covering anything. The rest of the components were placed according to the routing. This process was done so that it wasn't as complex to route while still staying in the size guidelines.

## Assemble Stage

 


Image 9. Front of the Physical Board Prior to Soldering



 


Image 10. Back of the Physical Board Prior to Soldering

 


Image 11. Front of the Physical Board After Soldering



Image 12. Back of the Physical Board After Soldering

Images 9-12 show the physical PCB after it arrived from shipment. The board before and after soldering are displayed. Every component was soldered on and then the board was tested by plugging it into the Arduino code that was written.

## **Enclosure Design**

 


Image 13. Drawing of the Top Piece

 


Image 14. Drawing of the Bottom Piece

 


Image 15. Drawing of the Full Enclosure

 


Image 16. PCB Enclosure

After designing the PCB, an enclosure was built so that the PCB had a place for storage. This was done using SolidWorks. There are two different parts, the top and bottom. An assembly was done so that the two parts could be mated together. There are five holes in the top so that

parts of the PCB will be displayed and accessed easily. This includes the 7-segment display, two buttons, a USB, and the buzzer. This is the current final design but there are always improvements that can be made to increase productivity. This could include holes in the bottom so the PCB can be mounted. Topics like this will be considered heavily before it gets 3D printed.